

LC\_Solver.nb by R. C. Toonen

Physical Electronics -- University of Akron -- Fall 2017

Replace {Cvmax value} with your calculated value.

Replace {Cvmin value} with your calculated value.

```
Cvmax = {Cvmax value}; (* maximum varactor capacitance, units = F *)

Cvmin = {Cvmin value}; (* minimum varactor capacitance, units = F *)

Cant = 8.19 * 10-12; (* antenna capacitance, units = F *)

f0mid = 1070 * 103; (* midband frequency, units = Hz *)

BW = 250 * 103; (* bandwidth, units = Hz *)

f0min = f0mid -  $\frac{BW}{2}$  (* minimum frequency, units = Hz *)

f0max = f0mid +  $\frac{BW}{2}$  (* maximum frequency, units = kHz *)

f0[L_, C_] :=  $\frac{1}{2 * \pi * \sqrt{L * C}}$  (* resonant frequency function *)

data = Solve[{f0min == f0[L, (C0 + Cvmax) + Cant], f0max == f0[L, (C0 + Cvmin) + Cant]}, {C0, L}];

C0 = 1012 * C0 /. data[[1, 1]] (* fixed capacitance, units = pF *)

L = 103 * L /. data[[1, 2]] (* inductance, units = mH *)
```